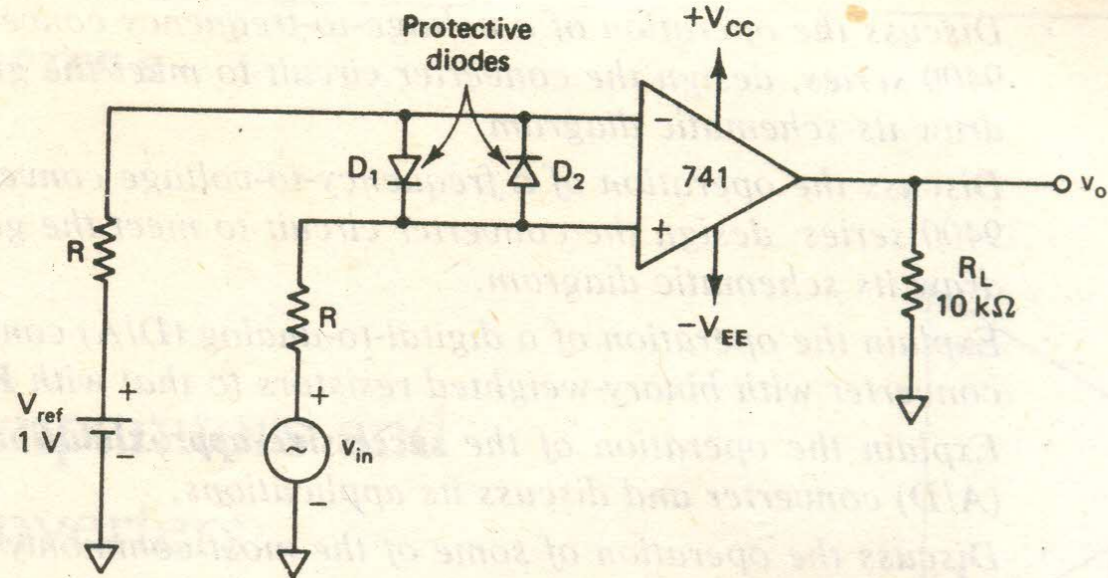



Electronics

Jimmy sebastian

Basic comparator



(a)

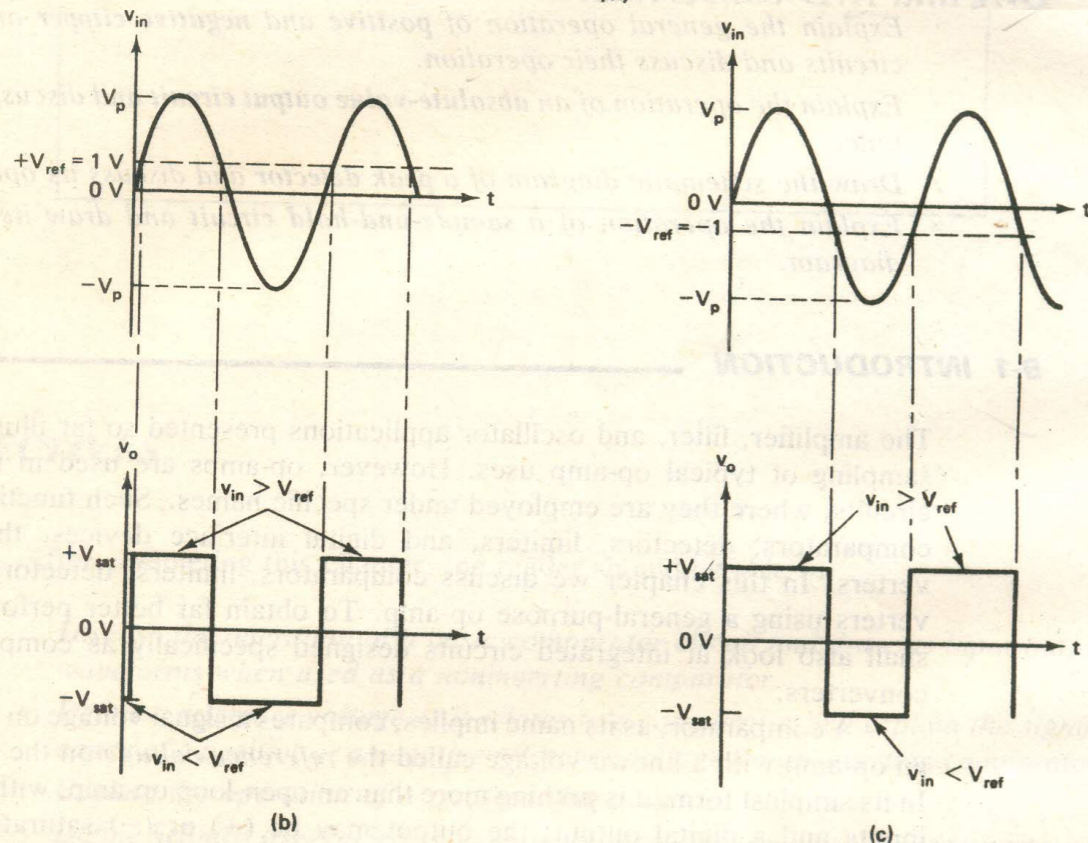

(b)

(c)

Figure 9-1 (a) Noninverting comparator and its input and output waveforms. (b) If V_{ref} is positive. (c) If V_{ref} is negative.

Noninverting comparator



A fixed reference voltage $V_{ref} = 1V$ is applied at (-) input and a time varying voltage V_{in} is applied at (+) input. It is also called Noninverting comparator

When v_{in} is less than V_{ref} the output voltage $V_0 = V_{sat} (-V_{EE})$ and When v_{in} is greater than V_{ref} the output voltage $V_0 = V_{sat} (+V_{CC})$

The diodes D_1 and D_2 are called clamp diodes They protect the opamp from damage due to excessive input voltage V_{in} . Because of these diodes the input difference voltage is clamped to either 0.7 or -0.7 V.

Inverting comparator

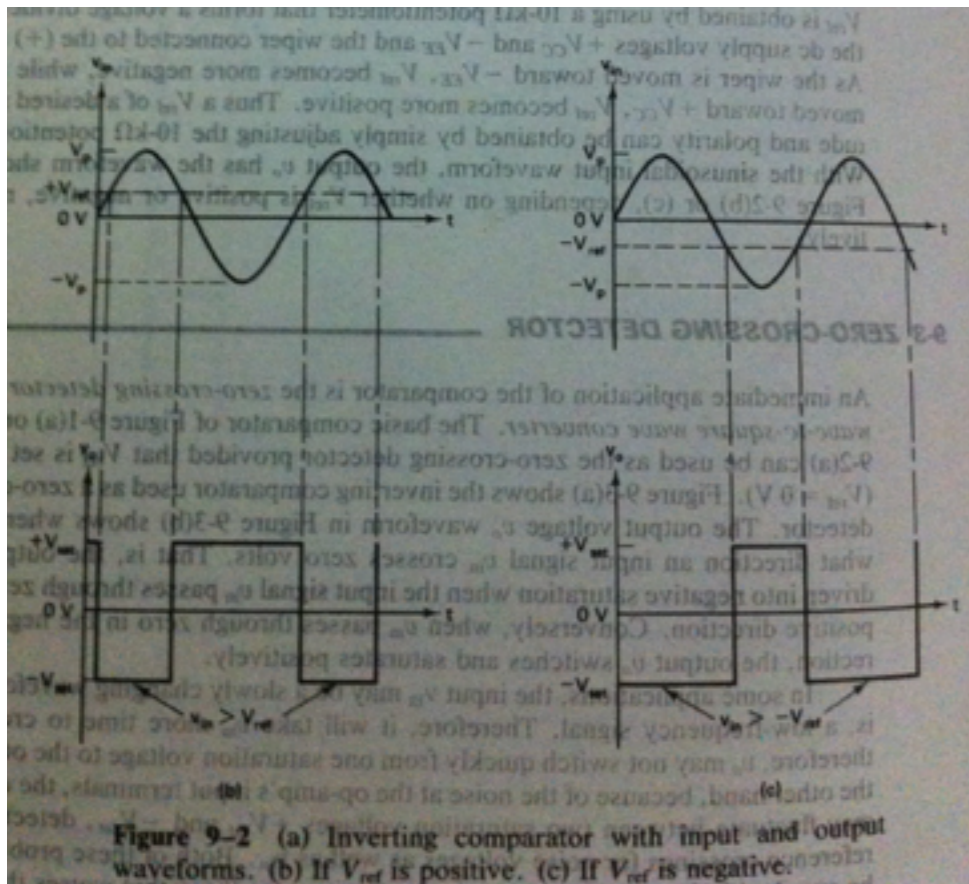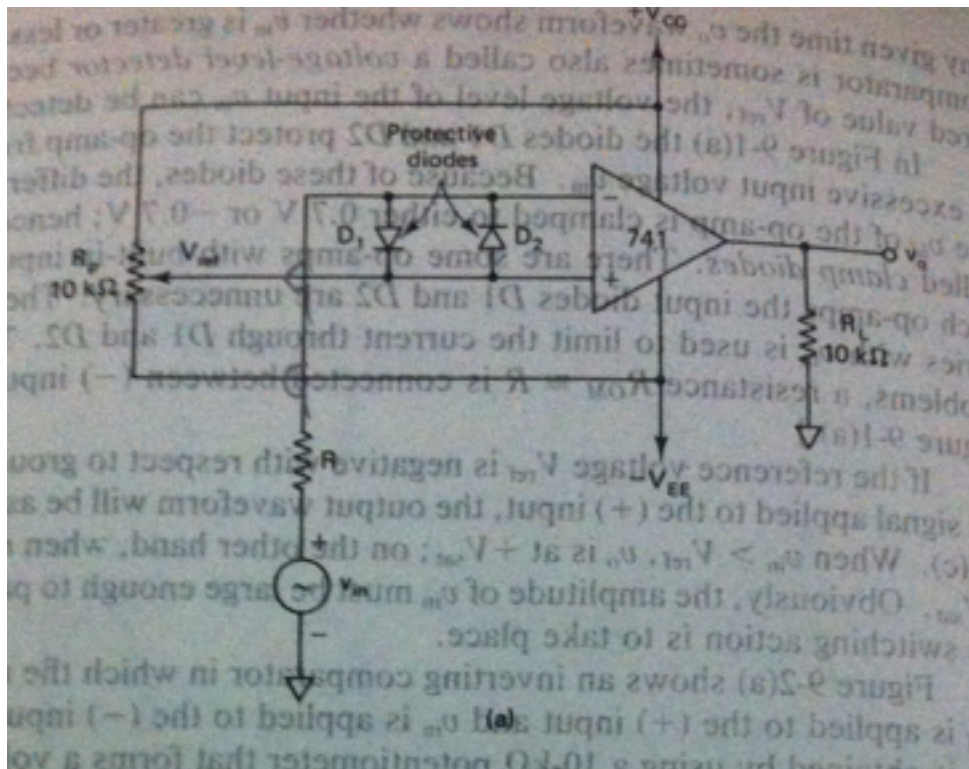A fixed reference voltage V_{ref} is applied at (+) input and a time varying voltage V_{in} is applied at (-) input. It is also called inverting comparator



Application of the comparator Zero crossing detector


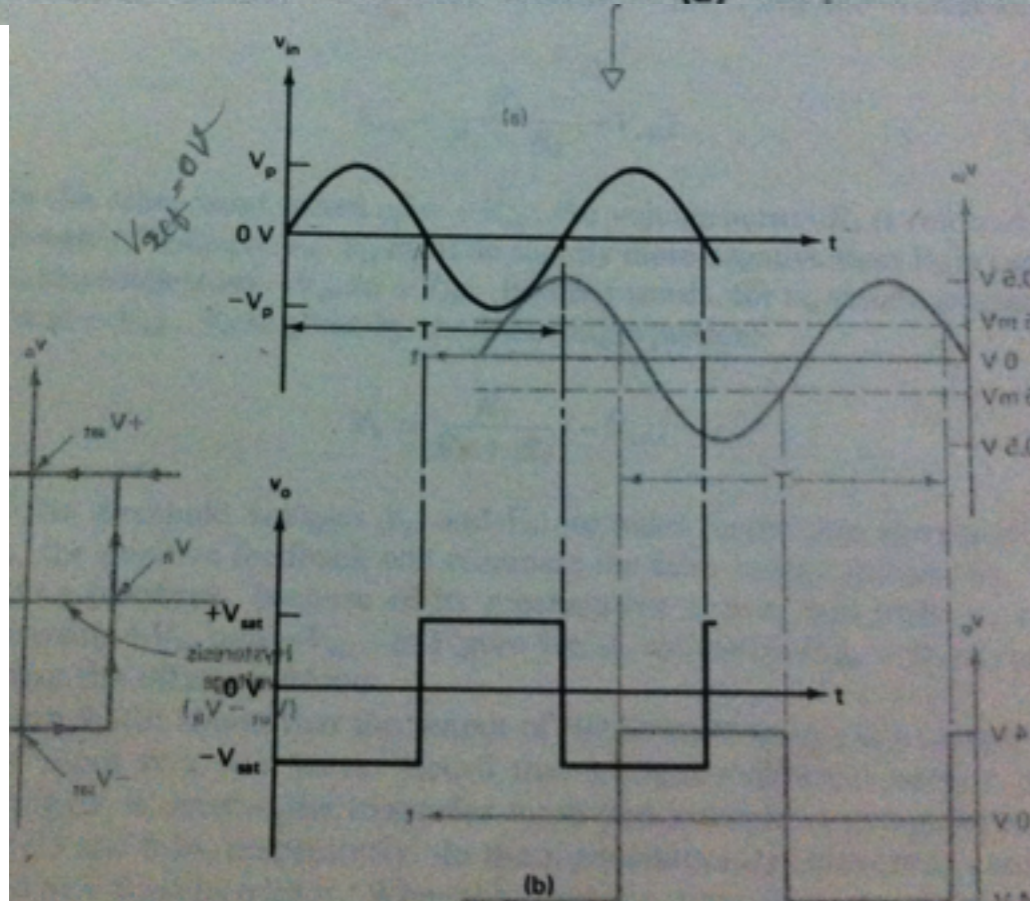
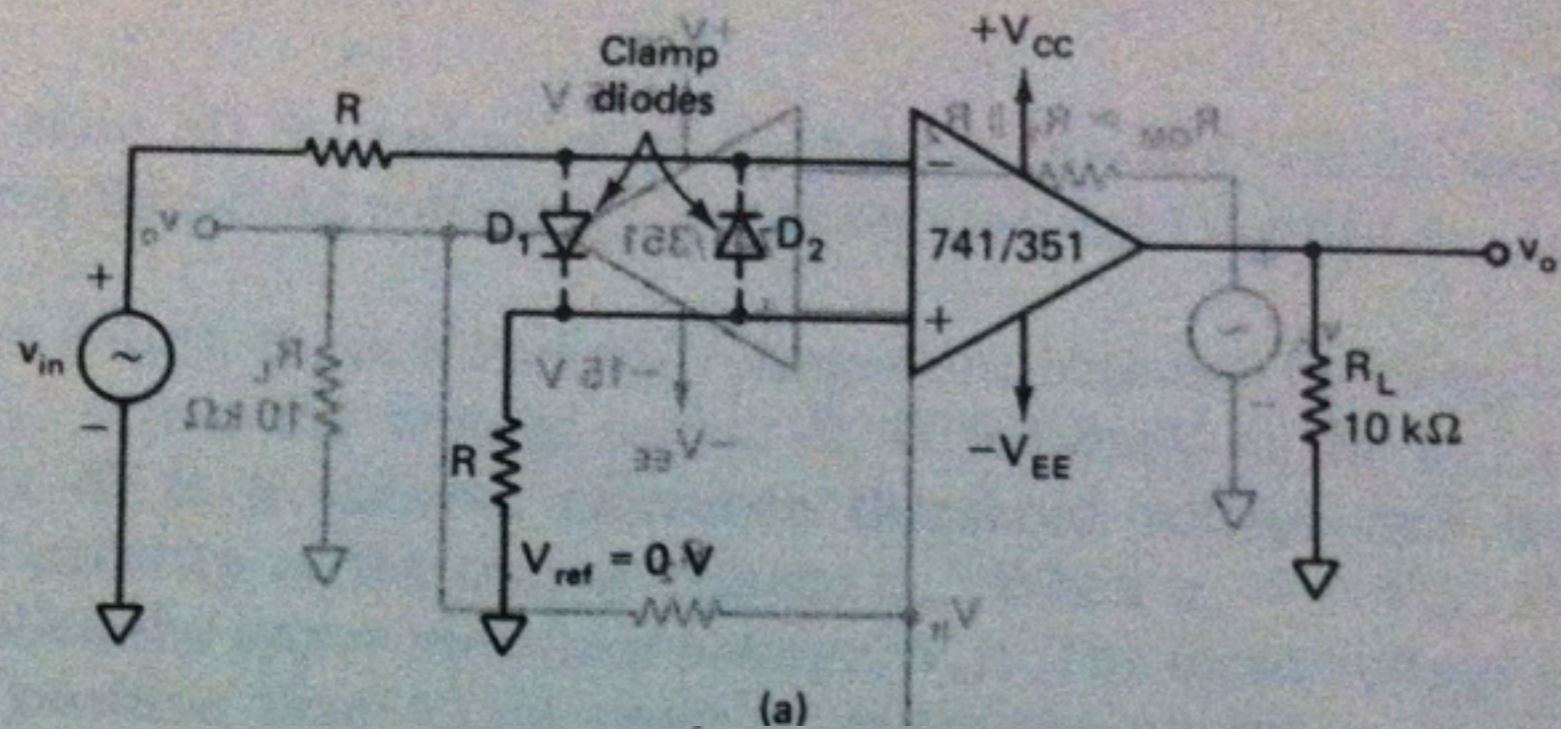


Figure 9-3 (a) Zero-crossing detector. (b) Its typical input and output waveforms.

The application of the comparator is a zero crossing detector or a sine wave to square wave converter. here V_{ref} is set to $0V$

The output V_0 is driven to negative saturation when input V_{in} crosses zero volts in the positive direction

Schmitt Trigger

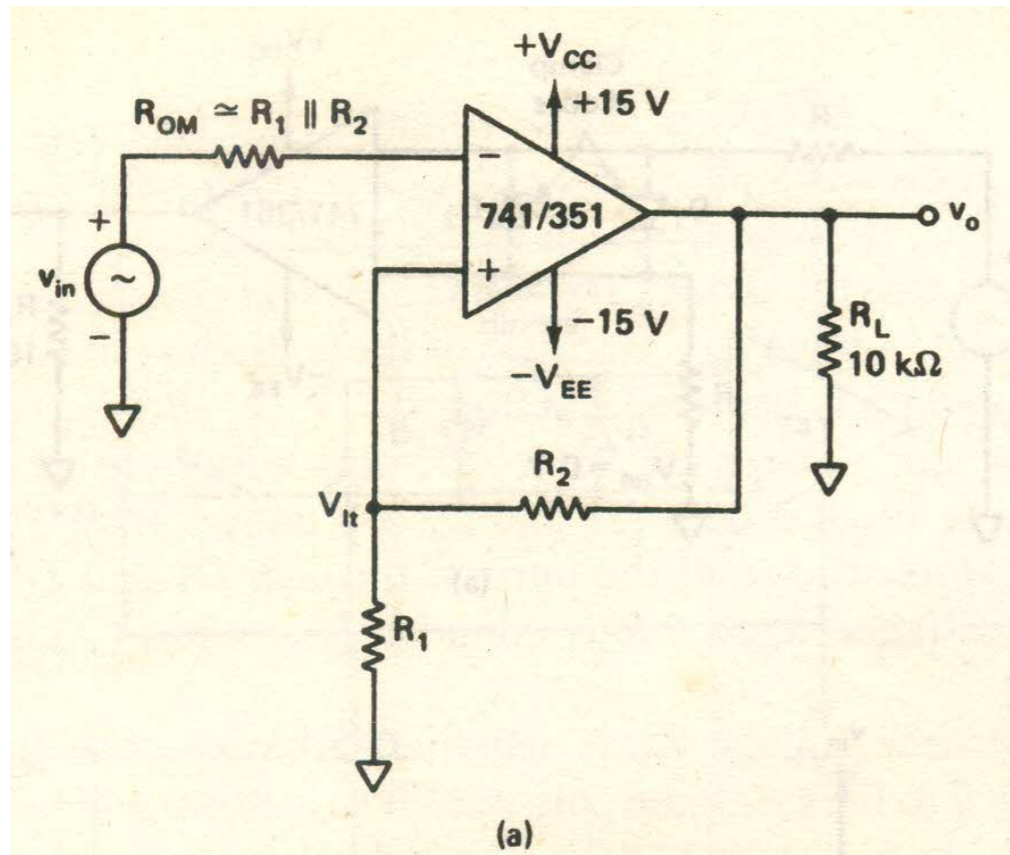

The circuit converts an irregular shaped waveform to a square wave or pulse. The input voltage v_{in} triggers the output v_o every time it exceeds certain voltage levels called upper threshold voltage V_{ut} and lower threshold voltage V_{lt} .

$$V_{ut} = \frac{R_1}{R_1 + R_2} (+V_{sat})$$

$$V_{lt} = \frac{R_1}{R_1 + R_2} (-V_{sat})$$


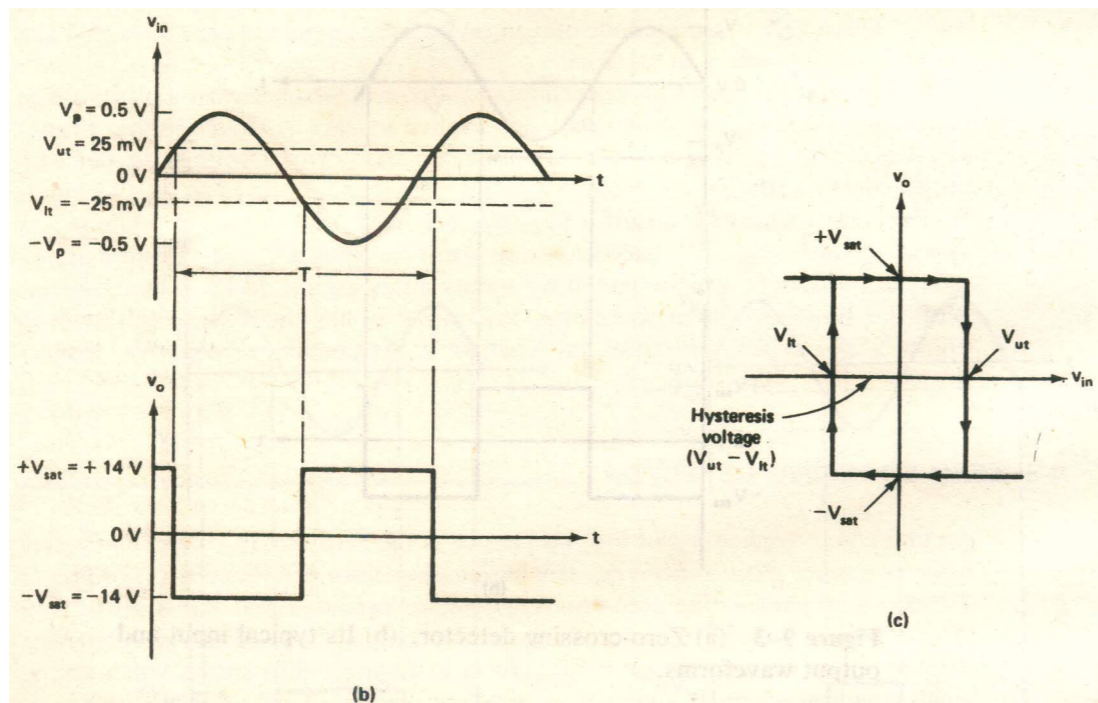


Figure 9-4 (a) Inverting comparator as Schmitt trigger. (b) Input and output waveforms of Schmitt trigger. (c) v_o versus v_{in} plot of the hysteresis voltage.

$$\begin{aligned} V_{hy} &= V_{ut} - V_{lt} \\ &= \frac{R_1}{R_1 + R_2} [+V_{sat} - (-V_{sat})] \end{aligned}$$

Digital to Analog converter

binary weighted resistors

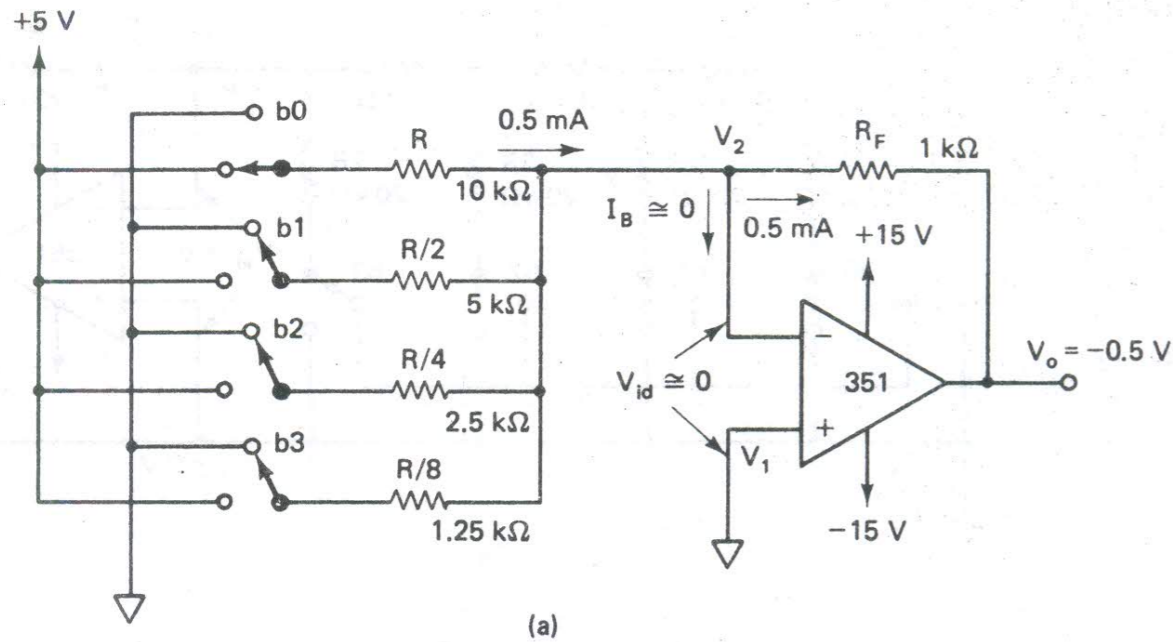

A D/A converter uses an opamp and either binary weighted resistors or R and 2R resistors.

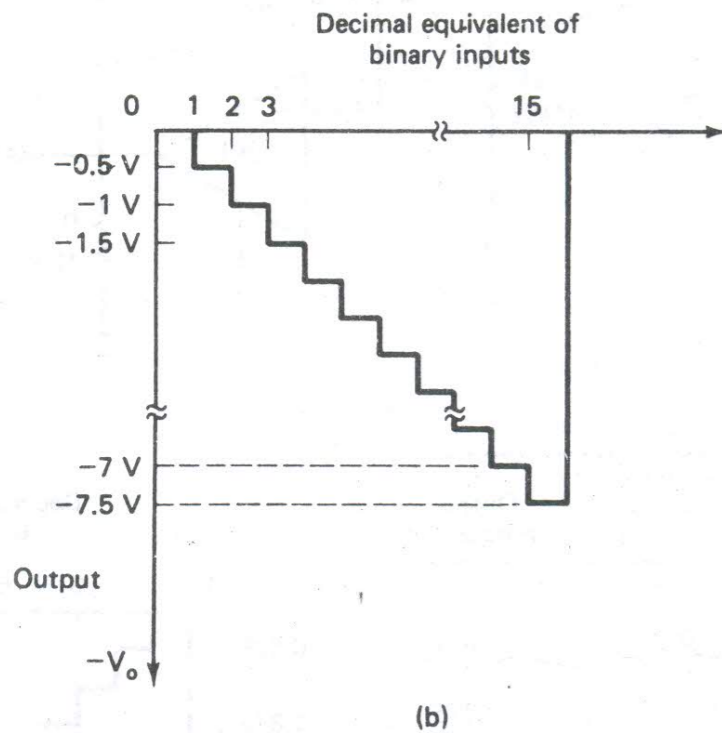


FIGURE 8-18 (a) D/A converter with binary-weighted resistors. (b) Graph of output versus inputs.

R and 2R resistors


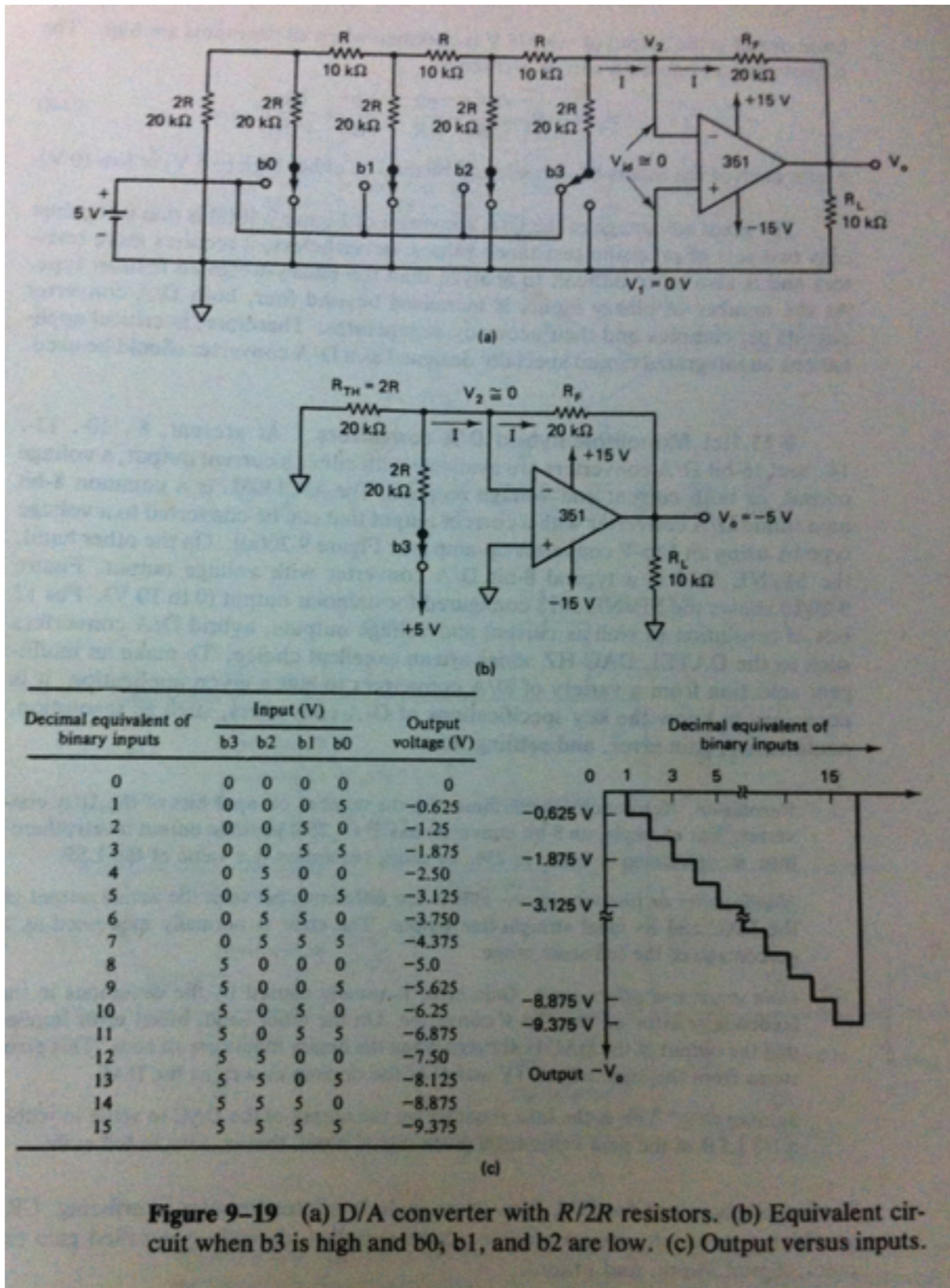


Figure 9-19 (a) D/A converter with $R/2R$ resistors. (b) Equivalent circuit when b_3 is high and b_0, b_1, b_2 are low. (c) Output versus inputs.

Analog to digital converter (A/D)

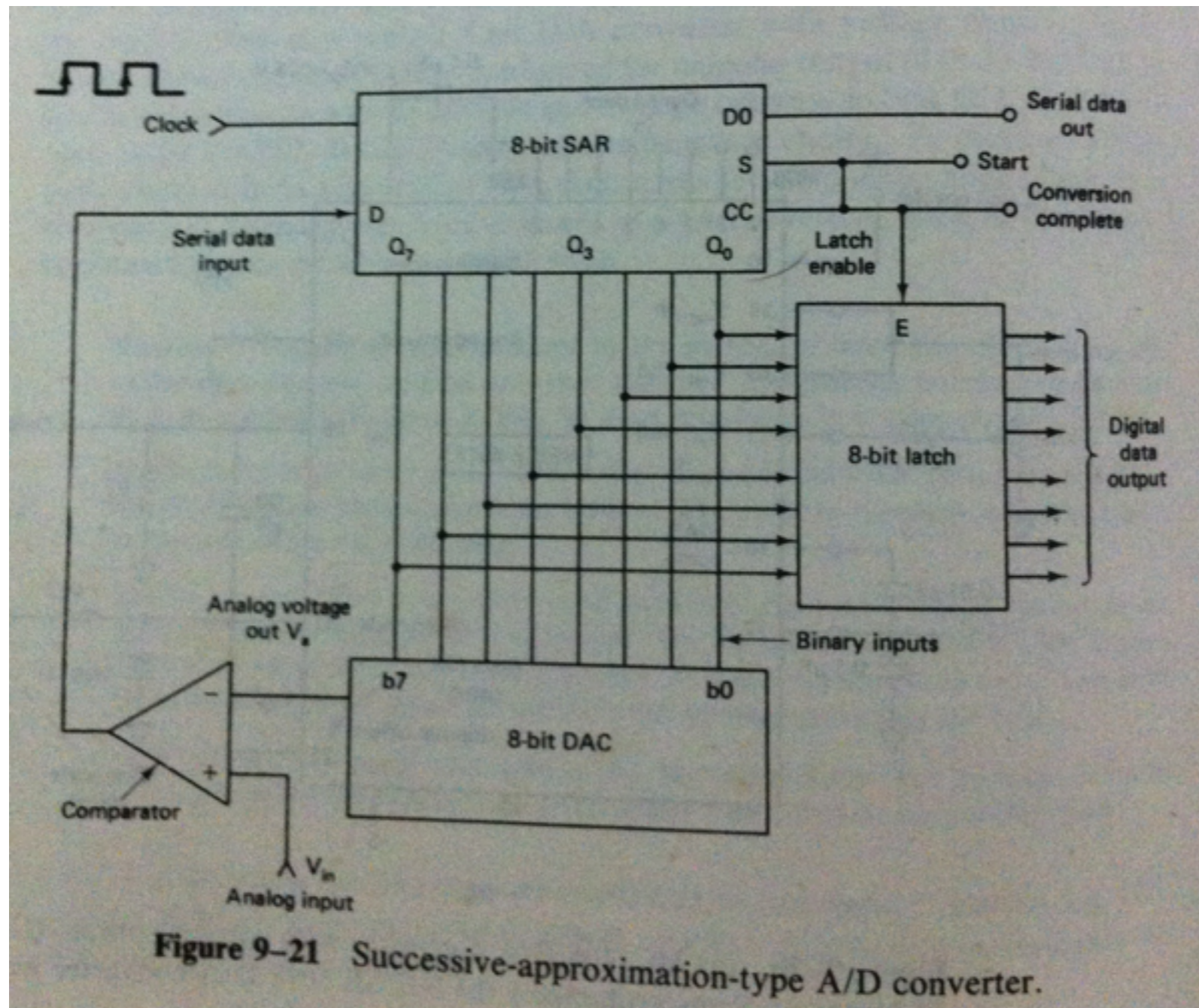

Peak Detector

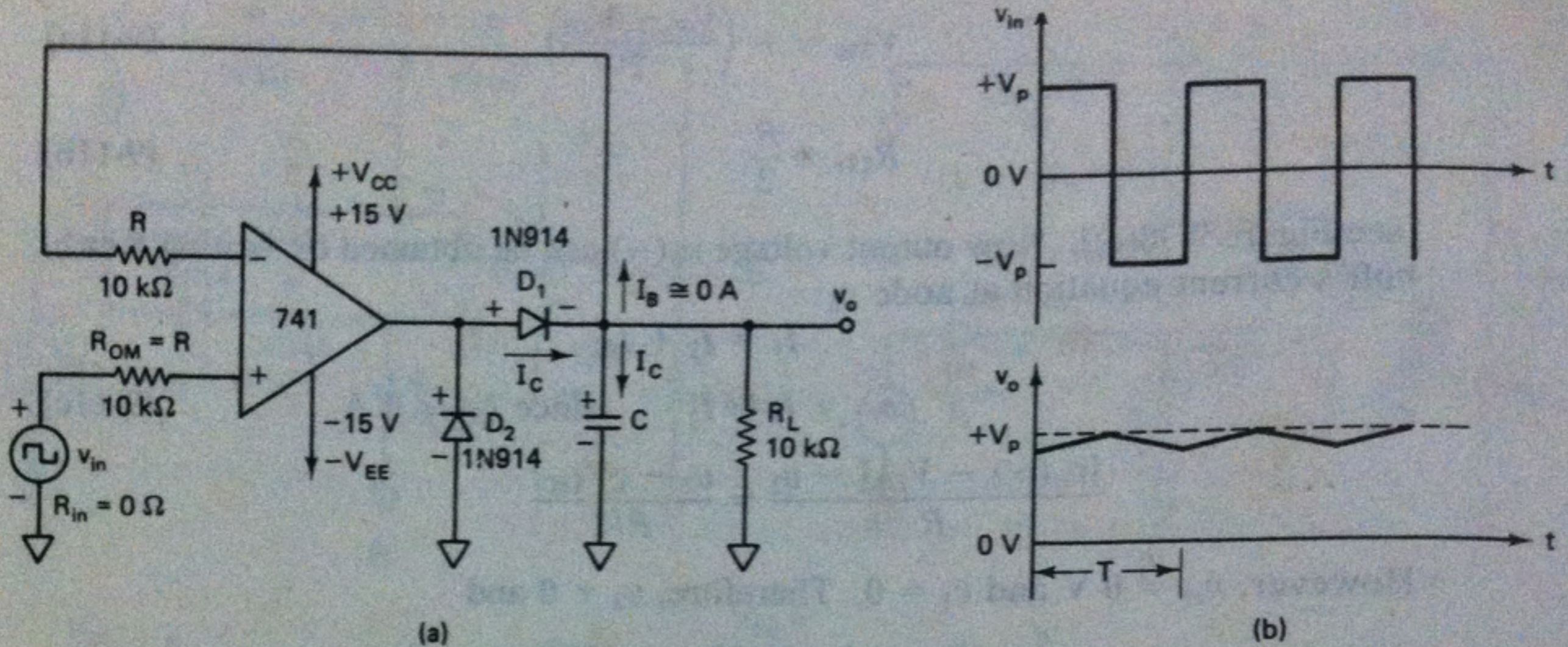


Figure 9-31 (a) Peak detector circuit. (b) Its input and output waveforms.

Sample and hold circuit

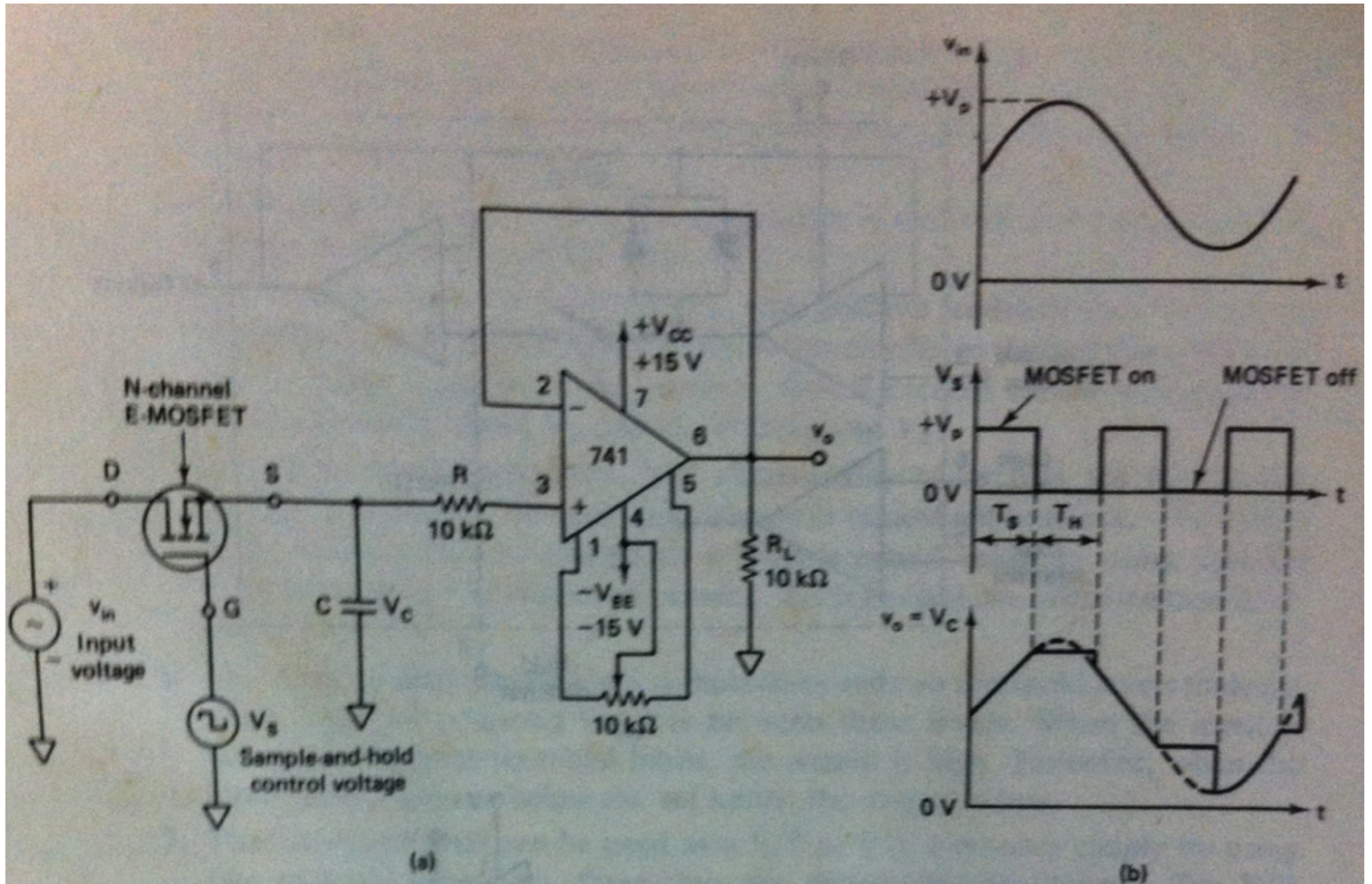


Figure 9-32 (a) Sample-and-hold circuit. (b) Its input and output waveforms.

IC555 timer internal architecture



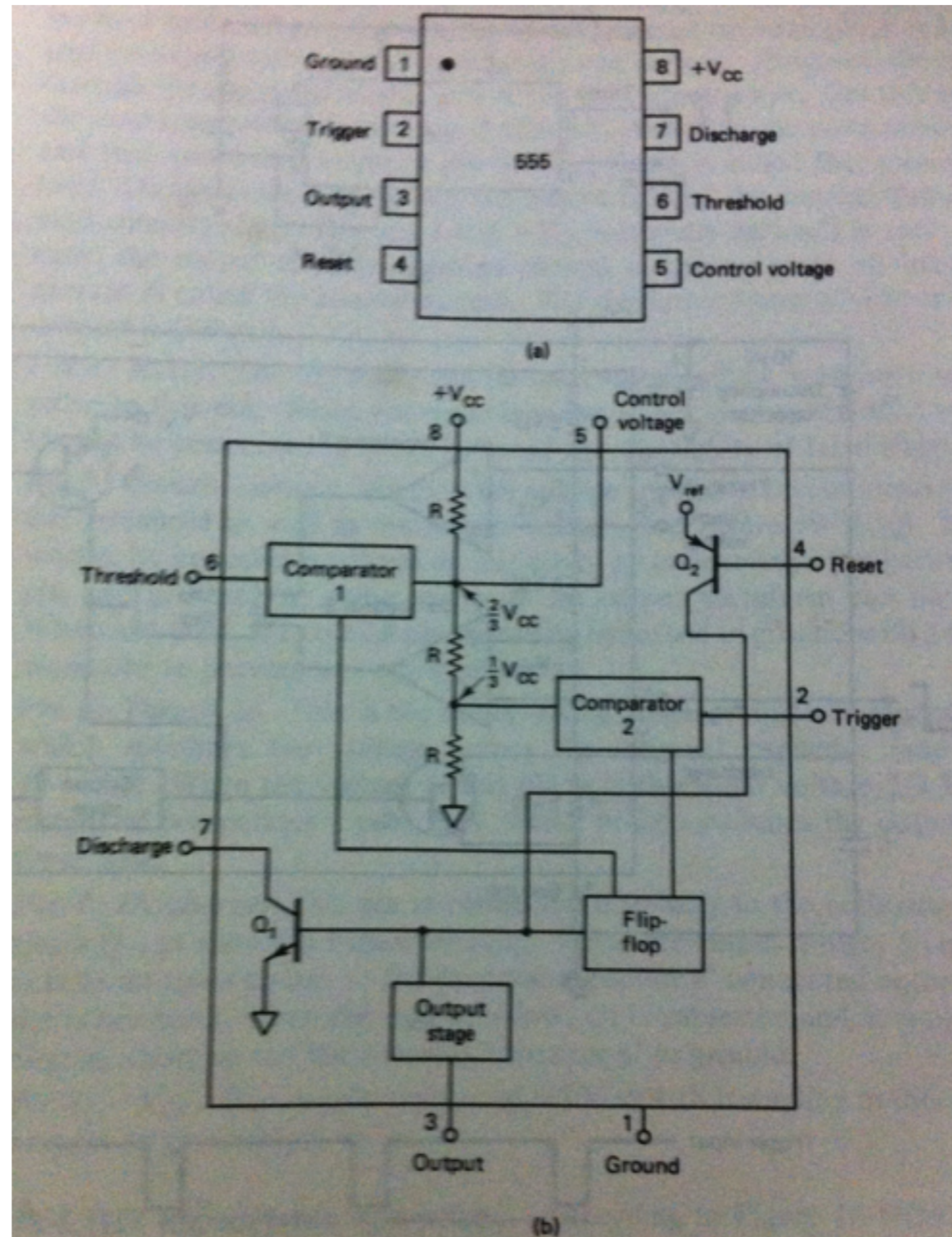
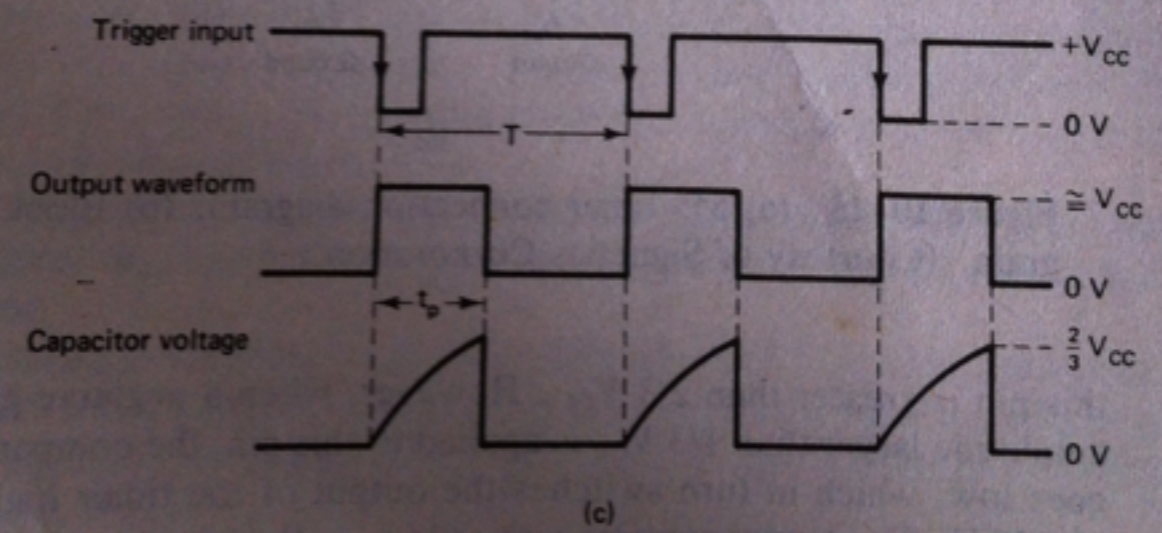
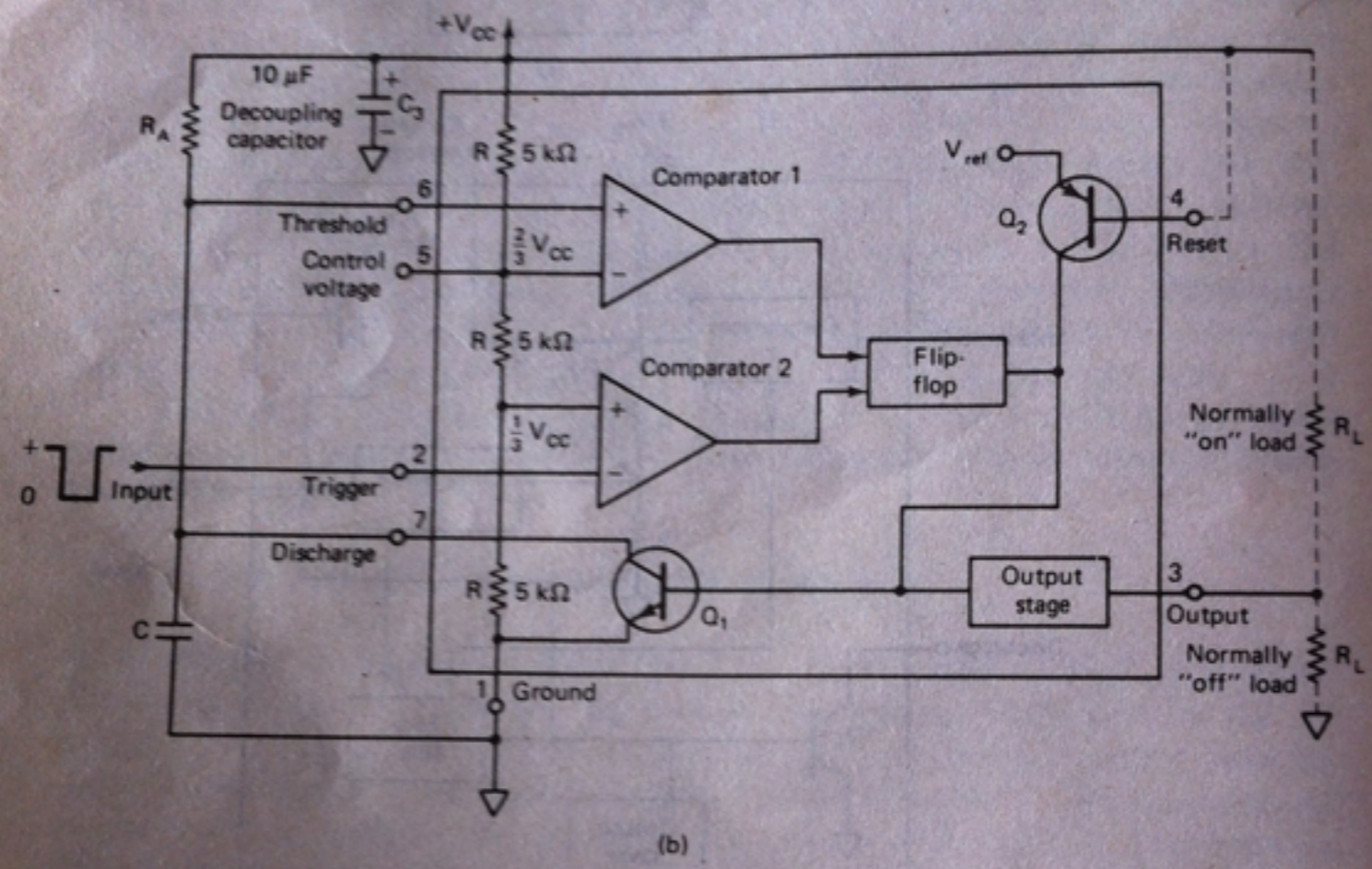


Figure 10-15 (a) 555 timer connection diagram. (b) Block dia-

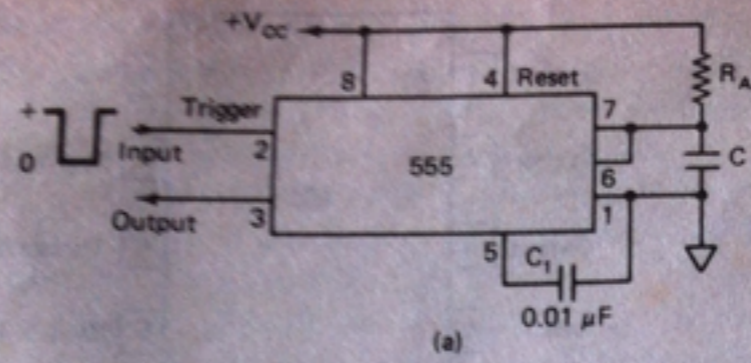

Phase Locked Loop

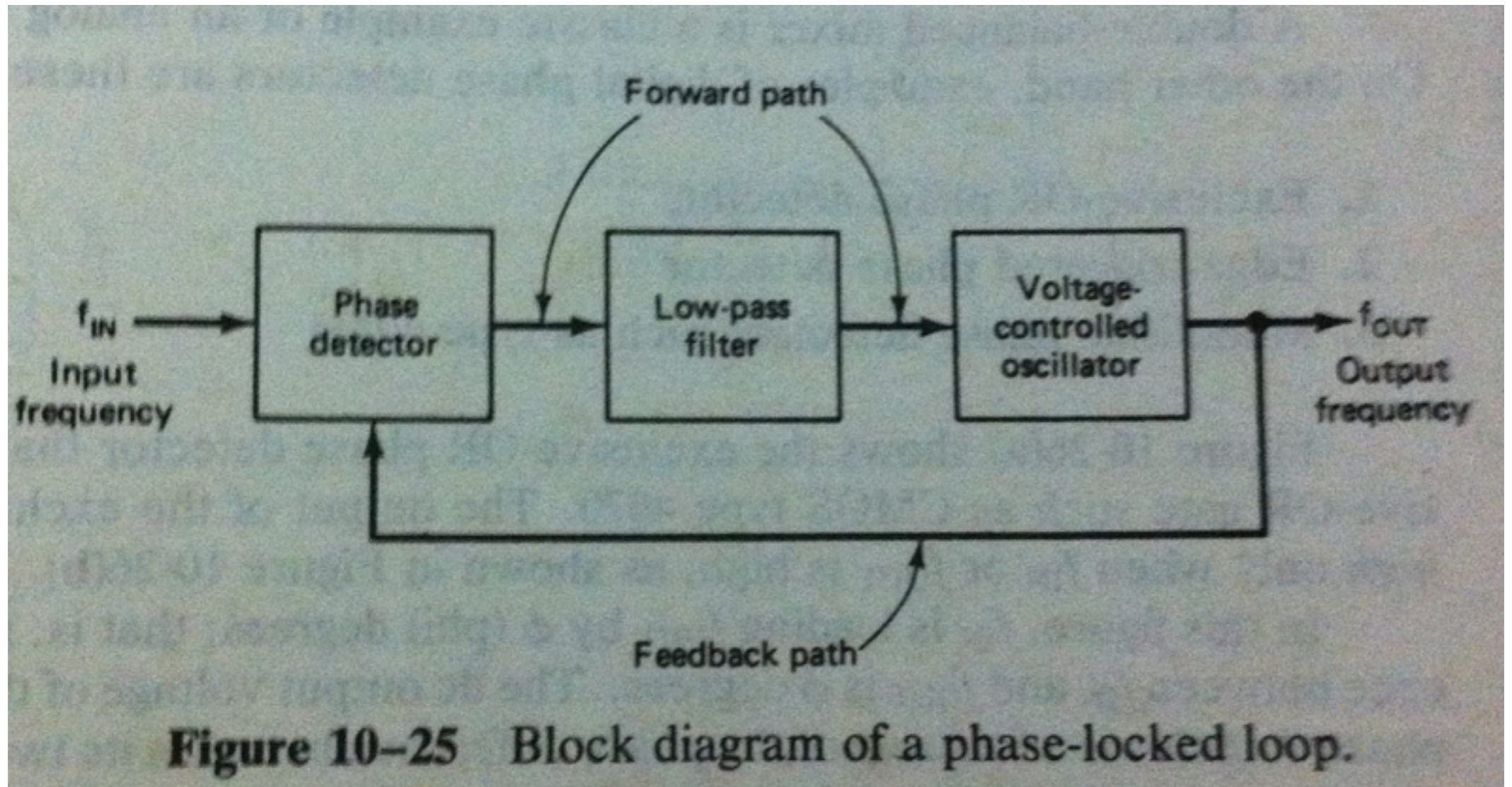

Applications IC565 - PLL Frequency Multiplier

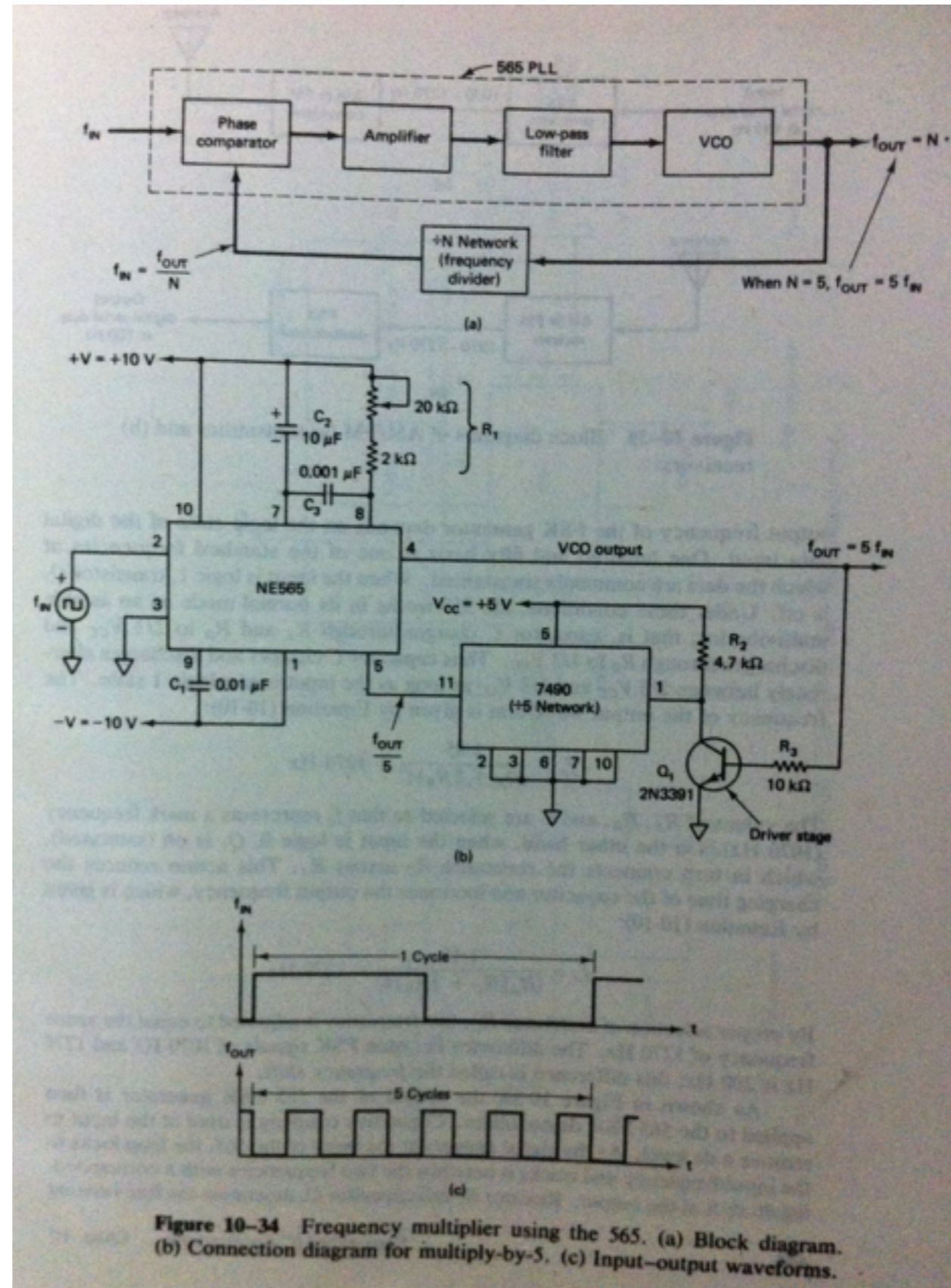


Figure 10-34 Frequency multiplier using the 565. (a) Block diagram. (b) Connection diagram for multiply-by-5. (c) Input-output waveforms.